

# Carry Lookahead Adder


Written by WJ Han

# problem

**How can you reduce the carry propagation time in a parallel adder.**

**Design four-bit adder with carry lookahead, the most widely used technique.**

# Full Adder Inside

 

Full adder with  $P$  and  $G$  shown

# carry propagation time

**The signal from the input carry  $C_i$  to the output carry  $C_{i+1}$  propagates through an AND gate and an OR gate, which constitute two gate levels.**

**The carry propagation time is an important attribute of the adder because it limits the speed with which two numbers are added.**

# carry lookahead

**One solution is to increase the complexity of the equipment in such a way that the carry delay time is reduced.**

**The most widely used technique employs the principle of carry lookahead logic.**

# carry output equation

$$C_{i+1} = G_i + P_i C_i$$

$$( P_i = A_i \oplus B_i, \quad G_i = A_i B_i )$$

$G_i$  is called a carry generate.

$P_i$  is called a carry propagate, because it determines whether a carry into stage  $i$  will propagate into state  $i+1$ .

each output carry

$$C_{i+1} = G_i + P_i C_i$$

$$C_1 = G_0 + P_0 C_0$$


$$C_2 = G_1 + P_1 C_1 = P_1 (G_0 + P_0 C_0)$$

$$= G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$C_3 = G_2 + P_2 C_2$$

$$= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$


# carry lookahead generator

 

Logic diagram of carry lookahead generator



# 4bit adder w. carry lookahead

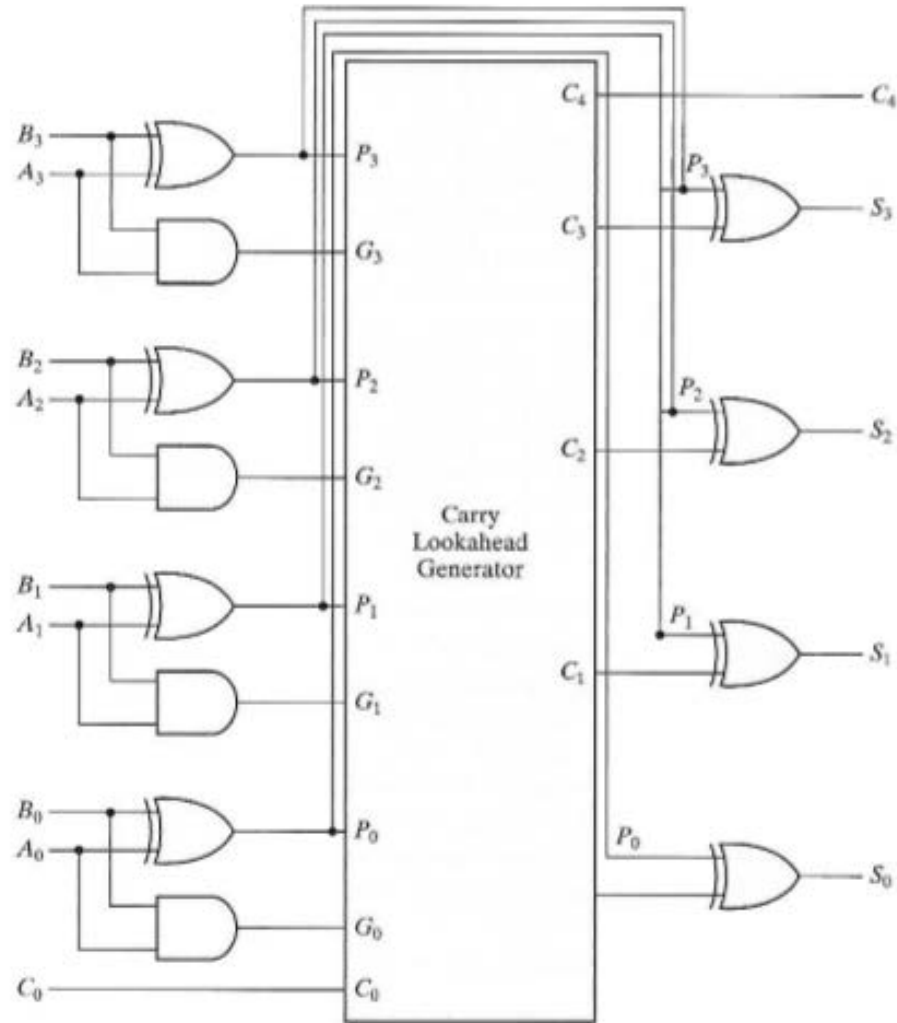

Four-bit adder with carry lookahead